

# Methodical Approximate Hardware Design and Reuse

Amir Yazdanbakhsh

**Bradley Thwaites**

Jongse Park

Hadi Esmaeilzadeh

Georgia Institute of Technology

# Outline

**Design** of approximate modules

Integration and **reuse** of approximate modules

**Safety** analysis


Output **quality** analysis

Questions

# Design Phase


- How does the designer specify what can be approximate?
  - Marking individual gates is burdensome.
  - Mark only output wires as approximate signals.
- Maintain Separation
- Approximation Plan and Interfacing

# Approximation Plan

 

```
module fa(a, b, c_in, c_out, s);  
  input a, b, c_in;  
  output c_out;  
  (*A*) output s;  
  wire w0, w1, w2, w3;  
  
  xor x0(w0, a, b);  
  xor x1(s, w0, c_in);  
  
  and u2(w1, a, b);  
  and u2(w2, a, c_in);  
  and u2(w3, b, c_in);  
  or u4(c_out, w1, w2, w3);  
endmodule
```

# Module Interfacing

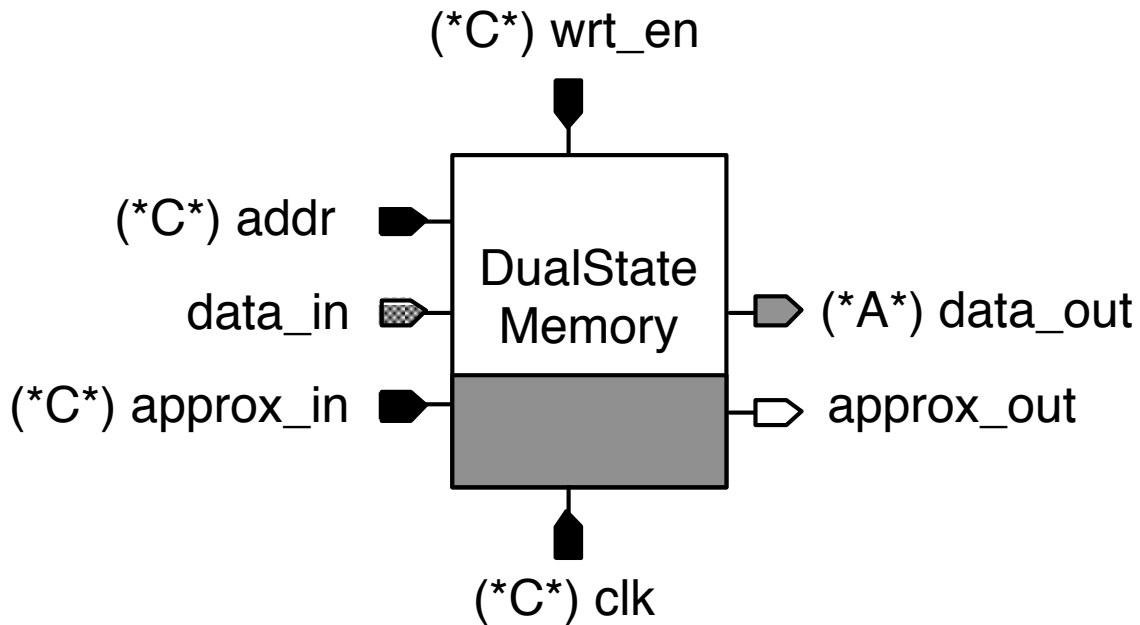


```
module DualStateMemory(  
    clk, wrt_en,  
    address,  
    data_in, approx_in,  
    data_out, approx_out);  
  
    (*C*) input clk;  
    (*C*) input wrt_en;  
    (*C*) input [N-1:0] address;  
    input [M-1:0] data_in;  
    (*C*) input approx_in;  
    (*A*) output [N-1:0] data_out;  
    output approx_out;  
    ...  
endmodule
```


# Reuse Phase

- Avoid rewriting modules from scratch
  - Ease of development
- Reuse of IP cores
  - Motivation for innovation and entrepreneurship
- Scalability for very large designs

# Overriding

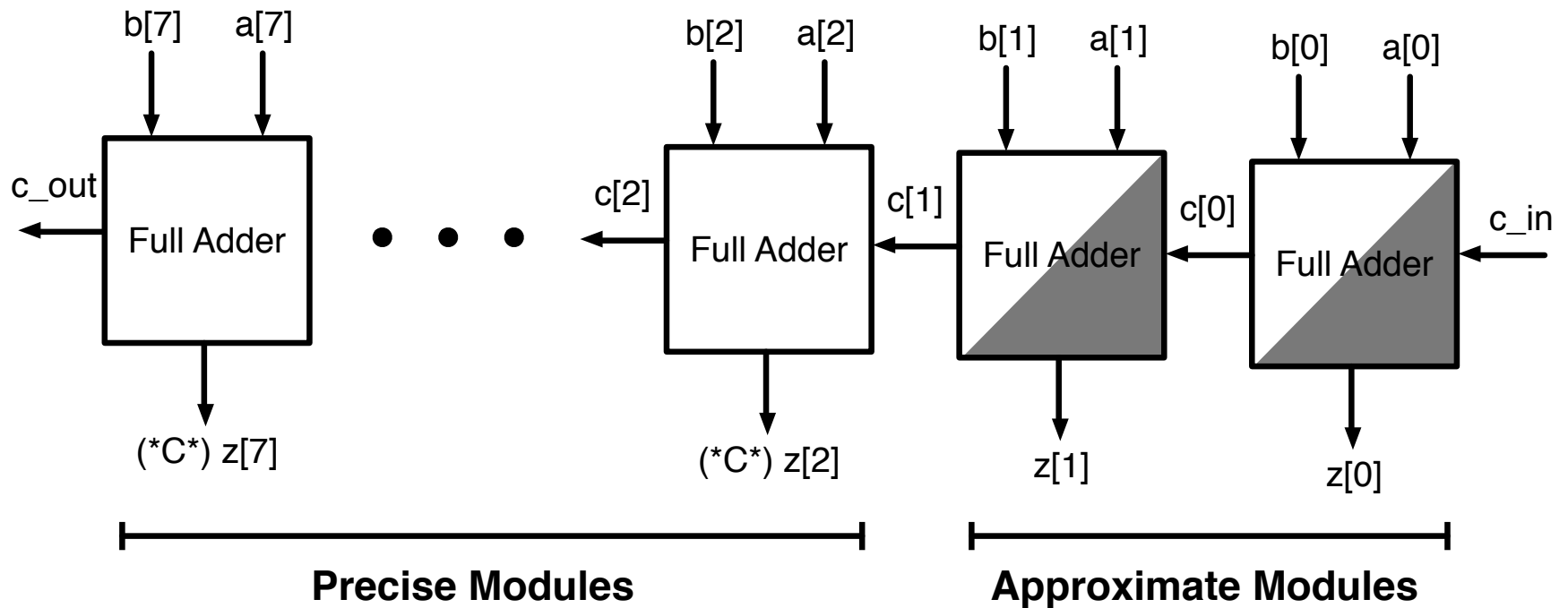


# Overriding within a Module

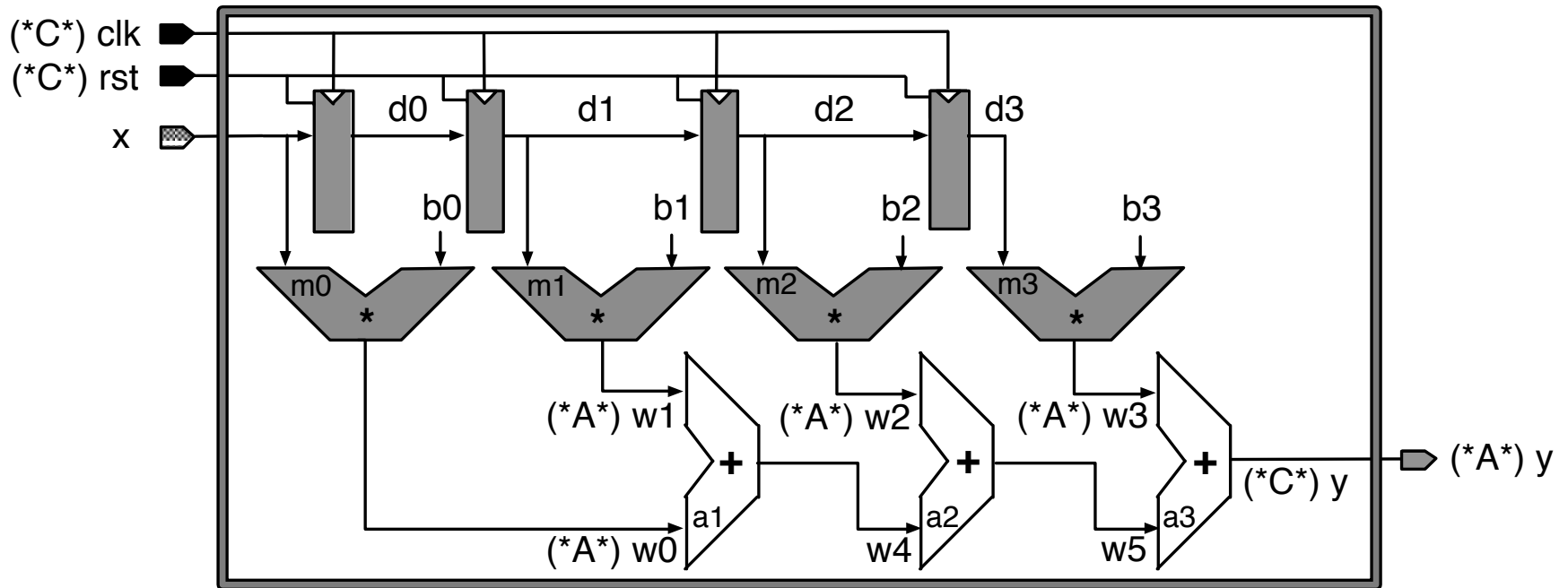



# Bridging

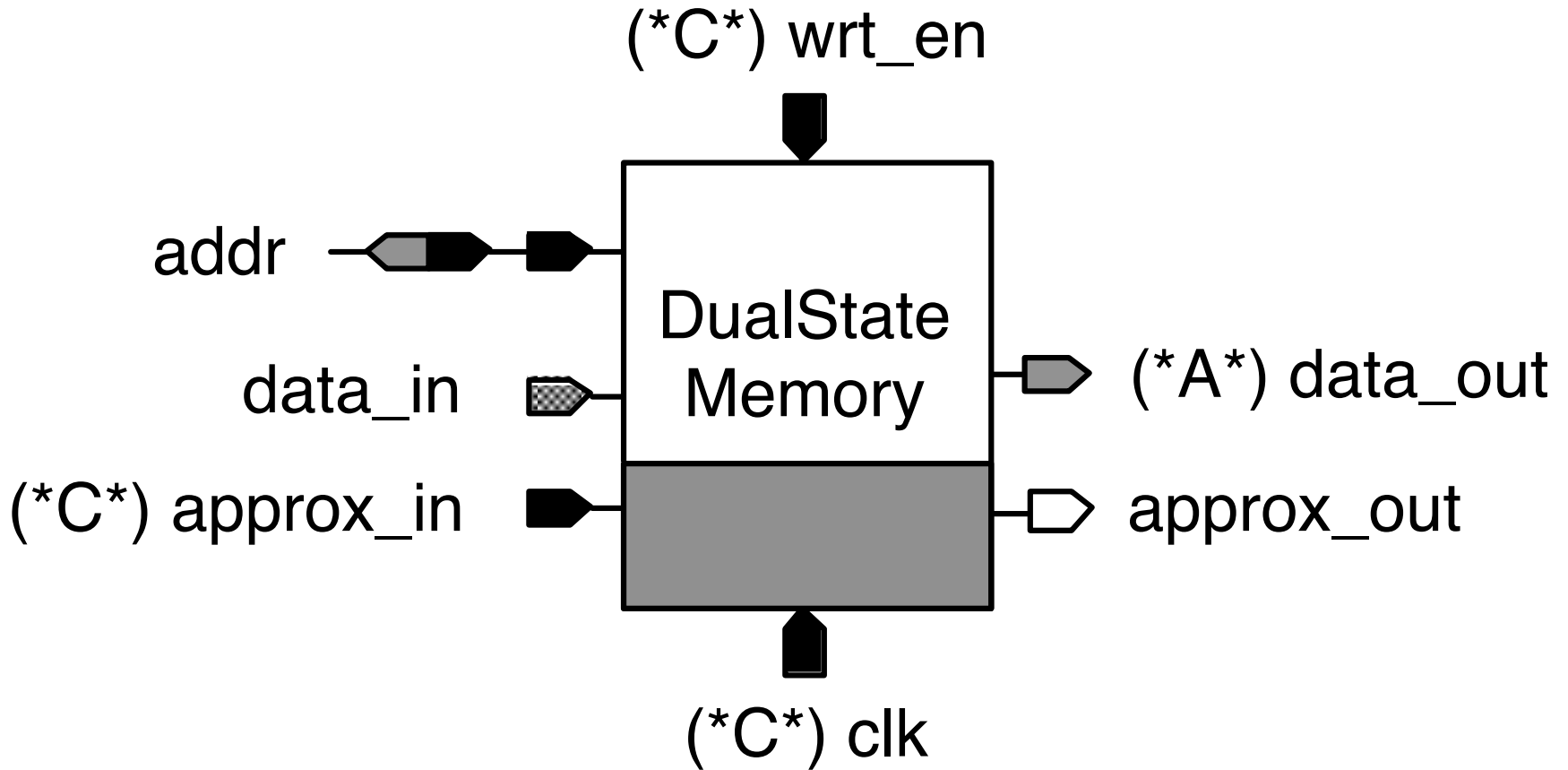

# Approximation Safety Analysis

- Approximation bridge vs. critical wire?
- Deciding final precision of all gates.
- Backward Slicing Algorithm

---

**Algorithm 1** Backward slicing to find precise wires.

---


**Inputs:**  $K$ : Circuit  
 $\Theta$ : Set of precise outputs  
 $\Psi$ : Set of critical wire overrides  
 $Y$ : Set of approximate wires overrides

**Output:**  $\mathfrak{R}$ : Set of precise wires

```
Initialize  $\mathfrak{R} \leftarrow \emptyset$ 
Initialize  $Q \leftarrow \emptyset$ 
for each  $w_i \in (\Theta \cup \Psi)$  do
  enqueue( $Q, w_i$ )
end for
while ( $Q \neq \emptyset$ ) do
   $w_i \leftarrow$  dequeue( $Q$ )
   $\Phi \leftarrow$  In  $K$ , find input wires of the gate that drives  $w_i$ 
  for each  $w_j \in \Phi$  do
    if ( $w_j \notin Y$  and  $w_j \notin \mathfrak{R}$ ) then
       $\mathfrak{R} \leftarrow \mathfrak{R} \cup w_j$ 
      enqueue( $Q, w_j$ )
    end if
  end for
end while
```

---

# Cone Analysis

 

# Quality Analysis

- Constraining approximation
- Safety vs. Quality
- ( $*A: f() < \epsilon^*$ )
- Profiling with test inputs
- Global confidence metric

# Questions?

